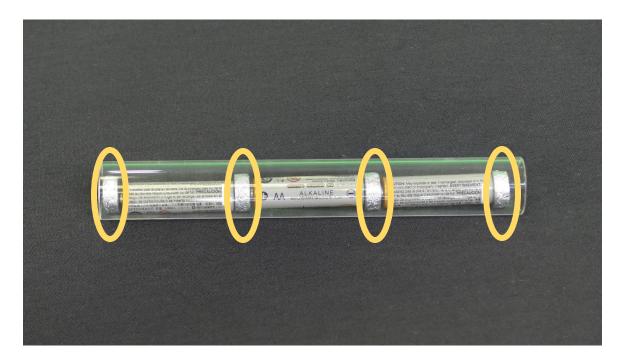







1. Use the tube to line up batteries and magnets.



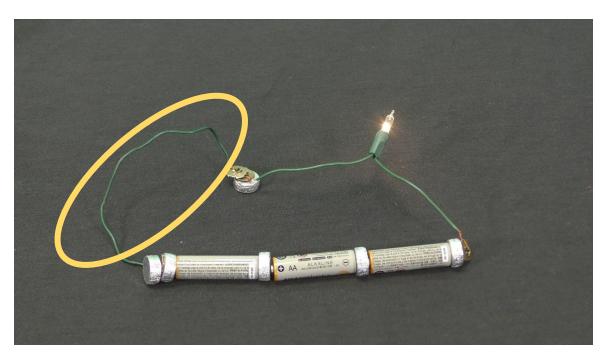
2. The extension wire can be used if the bulb wire is too short.







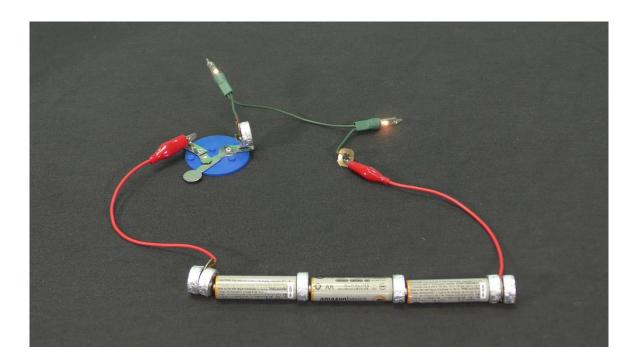3. Use the alligator clips to connect the switch as well as the motor.



4. For a better connection you can try using an extra magnet.

